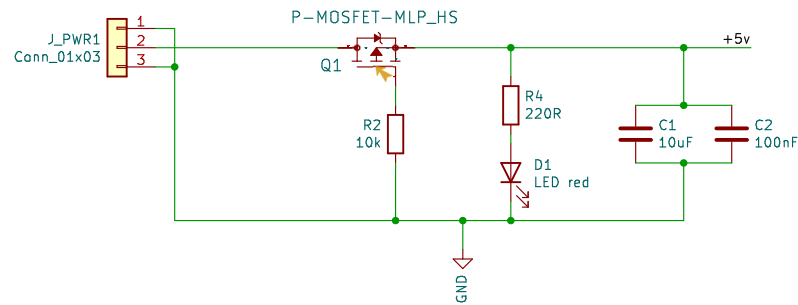


Common Power Supply (where applicable)




PB171 Project


CPU: ATmega2560-16A

BASIC SCHEMATICS

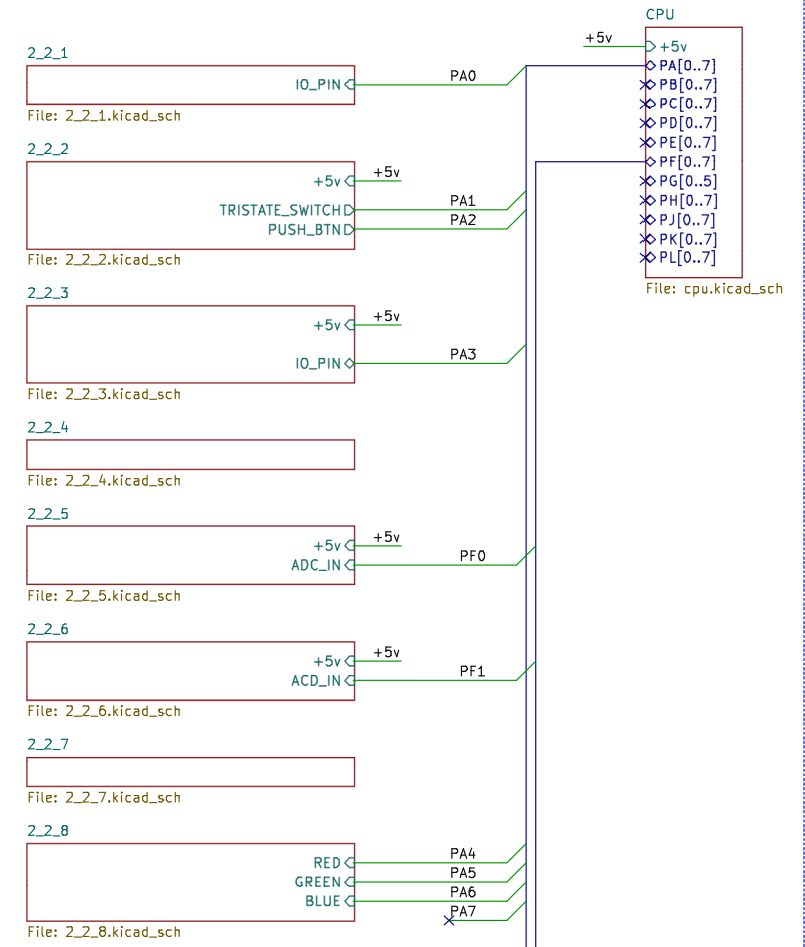
The following exercises were connected to a single CPU, where applicable.



HIGH POWER CONSUMPTION

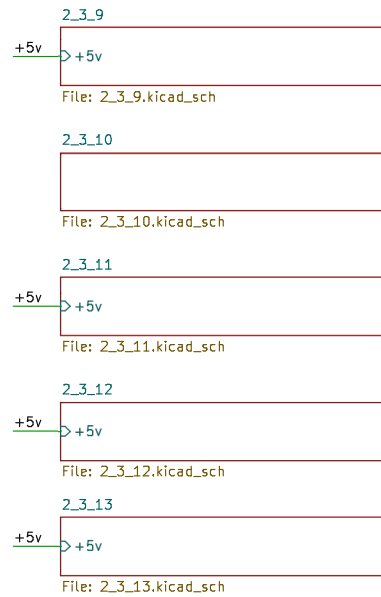

PERIPHERALS

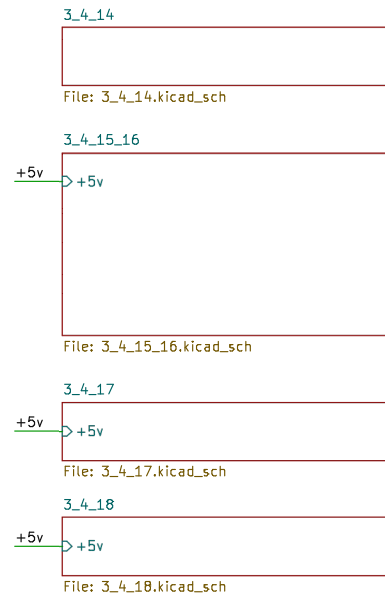

The power supply is 5 V.
Please specify a link to the datasheet of the used LED and the used CPU.


Sheet: /
File: hw.kicad_sch

Title: PB171: Assignment

Size: A4 Date: 2021-04-07
KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32

Rev: 1
Id: 1/19

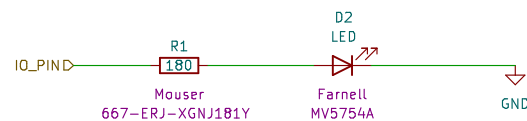Draw schematics of the circuit with one LED driven by the CPU. The power supply is 5 V. Please specify a link to the datasheet of the used LED and the used CPU.



At standard temperature (25deg C):

[1; p.355]: Voltage on any Pin except RESET with respect to Ground: $-0.5V$ to $VCC+0.5V$.
[1; p.355]: DC Current per I/O Pin: $40.0mA$

Assuming $VCC = 5V$, the upper voltage bound on PA0 is $5.5V$.

[2; p.3]: LED Diode Continuous Forward Current: $20.0mA$
[2; p.3]: LED Diode Forward Voltage: typical $2V$, maximum $2.5V$

$$R = (V_{PA0} - V_F) / I_F = (5.5 - 2) / 0.020 = 175 \text{ Ohm}$$

At the same time, the maximum amount of power that can enter the resistor is $5.5V \cdot 0.0040A = 0.022 \text{ W}$, so we'd need a resistor with a power rating of ca $1/40W$ or higher.

[1] <https://ww1.microchip.com/downloads/en/DeviceDoc/ATmega640-1280-1281-2560-2561-Datasheet-DS40002211A.pdf>
[2] <http://www.farnell.com/datasheets/1498852.pdf>

Regarding the data-sheet of the ATmega2560, each I/O port is tested with $20mA$.

The maximum current for the combination of port registers is the following:

J0-J7 + A0-A7 + G2 < $200mA$
C0-C7 + G0-G1 + D0-D7 + L0-L7 < $200mA$
G3-G4 + B0-B7 + H0-B7 < $200mA$
E0-E7 + G5 < $100mA$
F0-F7 + K0-K7 < $100mA$

Sheet: /2_2_1/
File: 2_2_1.kicad_sch


Title: Basic Schematic 1

Size: A4
KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32

Date:
Id: 2/19

Rev:

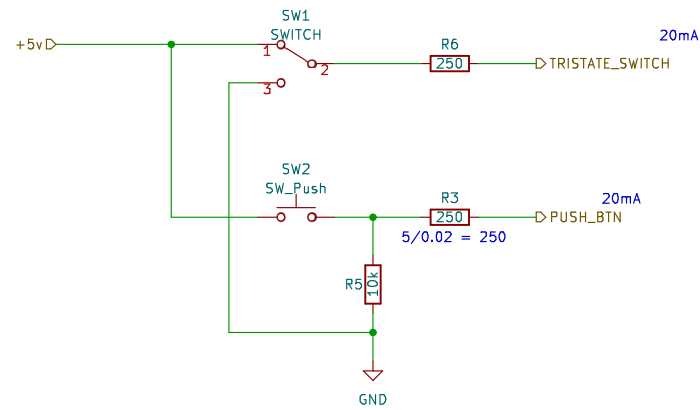Draw schematics of the circuit with one switch and one button connected to the CPU as two input devices connected to two separate pins.




Sheet: /2_2_2/
File: 2_2_2.kicad_sch

Title: Basic Schematic 2

Size: A4 Date:
KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32

Rev:
Id: 3/19

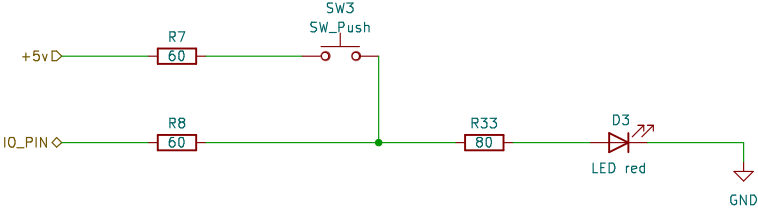Draw schematics of the circuit with one button and one LED connected to any IO pin on the CPU.
If the IO pin is set as output, the LED is driven by the CPU.
If the IO pin is set as input, the CPU is able to read the state of the button and the LED indicates the state of the button, too.



Sheet: /2_2_3/
File: 2_2_3.kicad_sch

Title: Basic Schematic 3

Size: A4	Date:	Rev:
KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32		Id: 4/19

PORTS

8-bit (except for G which is 6-bit) bi-directional I/O port with internal pull-up resistors (selected for each bit).

The port output buffers have symmetrical drive characteristics with both high sink and source capability.



As inputs, port pins that are externally pulled low will source current if the pull-up resistors are activated.

The port pins are tri-stated when a reset condition becomes active, even if the clock is not running.

Ports F and K serve as analog inputs to the ADC, or as an 8-bit bi-directional I/O port, if the ADC is not used.

If the JTAG interface is enabled, the pull-up resistors on pins PF7(TDI), PF5(TMS), and PF4(TCK) will be activated even if a reset occurs.

Port F also serves the functions of the JTAG interface.

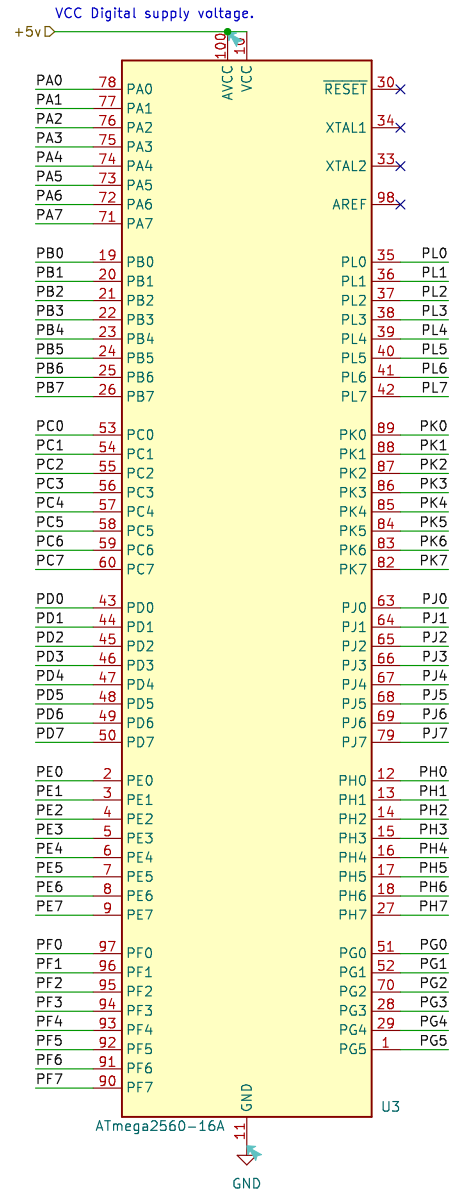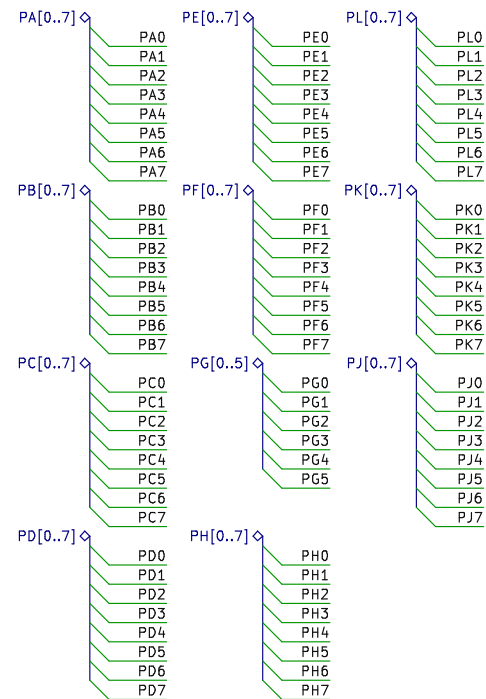

ATmega2560-16A

Sheet: /CPU/
File: cpu.kicad_sch

Title: Basic Schematics Shared CPU

Size: A4 Date:
KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32

Rev:
Id: 5/19

+5v VCC Digital supply voltage.

PA0 78	PA0	RESET 30
PA1 77	PA1	
PA2 76	PA2	XTAL1 34
PA3 75	PA3	
PA4 74	PA4	XTAL2 33
PA5 73	PA5	
PA6 72	PA6	AREF 98
PA7 71	PA7	
PB0 19	PB0	PL0 35
PB1 20	PB1	PL1 36
PB2 21	PB2	PL2 37
PB3 22	PB3	PL3 38
PB4 23	PB4	PL4 39
PB5 24	PB5	PL5 40
PB6 25	PB6	PL6 41
PB7 26	PB7	PL7 42
PC0 53	PC0	PK0 89
PC1 54	PC1	PK1 88
PC2 55	PC2	PK2 87
PC3 56	PC3	PK3 86
PC4 57	PC4	PK4 85
PC5 58	PC5	PK5 84
PC6 59	PC6	PK6 83
PC7 60	PC7	PK7 82
PD0 43	PD0	PJ0 63
PD1 44	PD1	PJ1 64
PD2 45	PD2	PJ2 65
PD3 46	PD3	PJ3 66
PD4 47	PD4	PJ4 67
PD5 48	PD5	PJ5 68
PD6 49	PD6	PJ6 69
PD7 50	PD7	PJ7 79
PE0 2	PE0	PH0 12
PE1 3	PE1	PH1 13
PE2 4	PE2	PH2 14
PE3 5	PE3	PH3 15
PE4 6	PE4	PH4 16
PE5 7	PE5	PH5 17
PE6 8	PE6	PH6 18
PE7 9	PE7	PH7 27
PF0 97	PF0	PG0 51
PF1 96	PF1	PG1 52
PF2 95	PF2	PG2 70
PF3 94	PF3	PG3 28
PF4 93	PF4	PG4 29
PF5 92	PF5	PG5 1
PF6 91	PF6	
PF7 90	PF7	

ATmega2560-16A

GND

U1

RESET 30

XTAL1 34

XTAL2 33

AREF 98

PL0 35

PL1 36

PL2 37

PL3 38

PL4 39

PL5 40

PL6 41

PL7 42

PK0 89

PK1 88

PK2 87

PK3 86

PK4 85

PK5 84

PK6 83

PK7 82

PJ0 63

PJ1 64

PJ2 65

PJ3 66

PJ4 67

PJ5 68

PJ6 69

PJ7 79

PH0 12

PH1 13

PH2 14

PH3 15

PH4 16

PH5 17

PH6 18

PH7 27

PG0 51

PG1 52


PG2 70

PG3 28

PG4 29

PG5 1

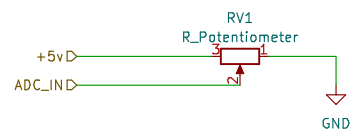Draw schematics of the circuit with one potentiometer connected as an analog input to the CPU. The CPU usually has several AD converters, you can use any of them.




Sheet: /2_2_5/
File: 2_2_5.kicad_sch

Title: Basic Schematic 5

Size: A4
KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32

Date:
Id: 7/19


Rev:

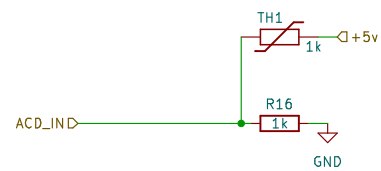

THERMISTOR PTC 1K OHM 1% 0603
<https://www.vishay.com/docs/33017/tfpt.pdf>
TFPT0603L1001FV



Sheet: /2_2_6/		
File: 2_2_6.kicad_sch		
Title: Basic Schematic 6		
Size: A4	Date:	Rev:
KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32		Id: 8/19

+5v VCC Digital supply voltage.

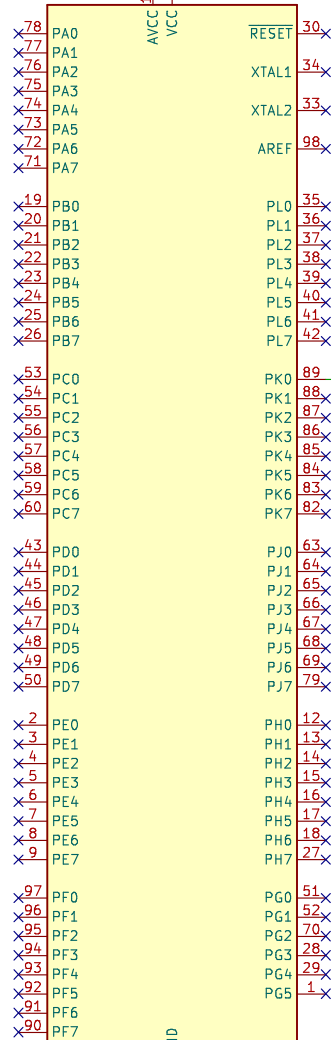

ATmega2560-16A

GND

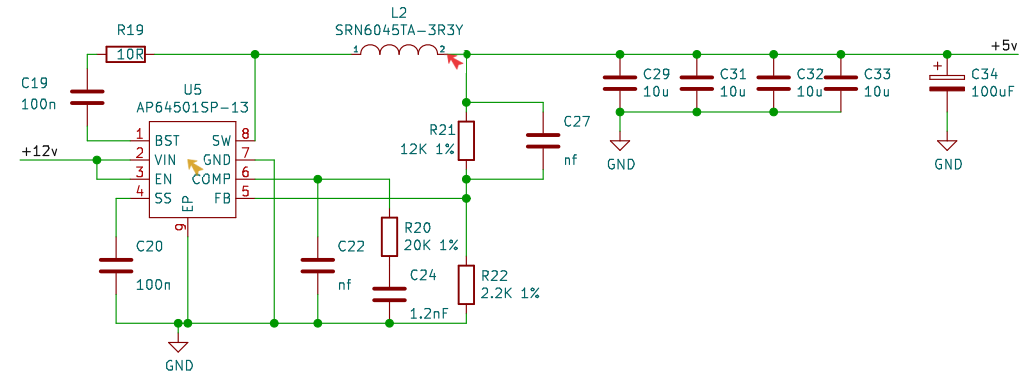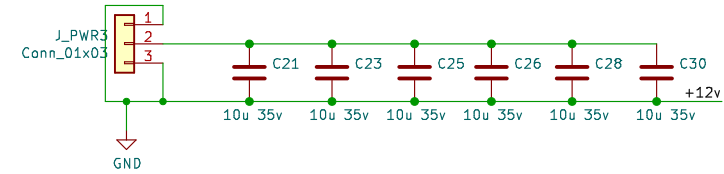

<https://www.diodes.com/assets/Datasheets/AP64501.pdf>

<https://search.murata.co.jp/Ceramy/image/img/A01X/G101/ENG/GRM155R71C104KA88-01.pdf>

<https://www.bourns.com/docs/Product-Datasheets/SRN6045TA.pdf>

https://tscdn.rohm.com/en/products/databook/datasheet/passive/resistor/chip_resistor/mcr-e.pdf

https://tscdn.rohm.com/en/products/databook/datasheet/passive/resistor/chip_resistor/mcr-e.pdf

<https://www.murata.com/en-global/products/productdetail.aspx?partno=GRM21BC8YA106ME11%23>

<https://cz.mouser.com/datasheet/2/315/ABE0000C49-947552.pdf>

Sheet: /2_2_7/

File: 2_2_7.kicad_sch

Title: Basic Schematic 7


Size: A4

Date:

KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32

Rev:

Id: 9/19

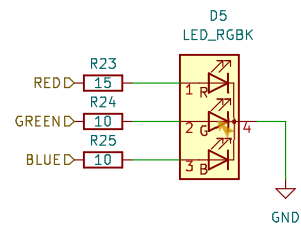


<https://docs.broadcom.com/docs/ASMG-PT00-DS100>


DC Forward Current 200mA
Forward Voltages (typical values at standard conditions):
Red V_f from 1.8, typical 2.2V, max 2.8V
 $R_r = (5V - 1.8V) / 0.2A = 16 \text{ ohm}$
 $R_r = (5V - 2.2V) / 0.2A = 14 \text{ ohm}$
 $R_r = (5V - 2.8V) / 0.2A = 11 \text{ ohm}$
Green V_f from 2.8, typical 3.1V, max 3.7V
 $R_r = (5V - 2.8V) / 0.2A = 11 \text{ ohm}$
 $R_r = (5V - 3.1V) / 0.2A = 9.5 \text{ ohm}$
 $R_r = (5V - 3.7V) / 0.2A = 6.5 \text{ ohm}$
Blue V_f from 2.8, typical 3.0V, max 3.7V
 $R_r = (5V - 2.8V) / 0.2A = 11 \text{ ohm}$
 $R_r = (5V - 3.0V) / 0.2A = 10 \text{ ohm}$
 $R_r = (5V - 3.7V) / 0.2A = 6.5 \text{ ohm}$

Sheet: /2_2_8/
File: 2_2_8.kicad_sch


Title: Basic Schematic 8

Size: A4	Date:	Rev:
KiCad E.D.A.	kicad 5.99.0-1.20210404git80728f8.fc32	Id: 10/19

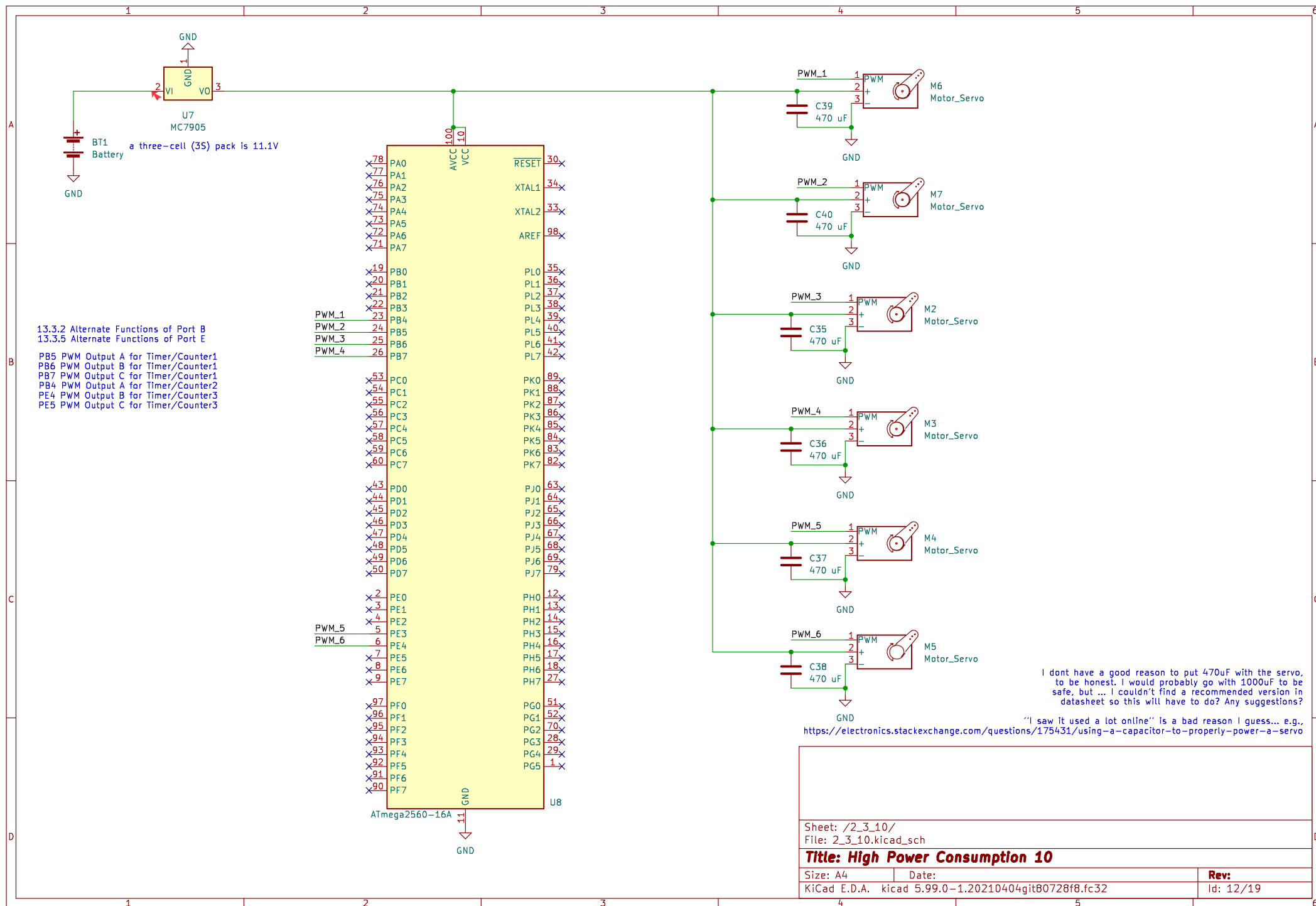

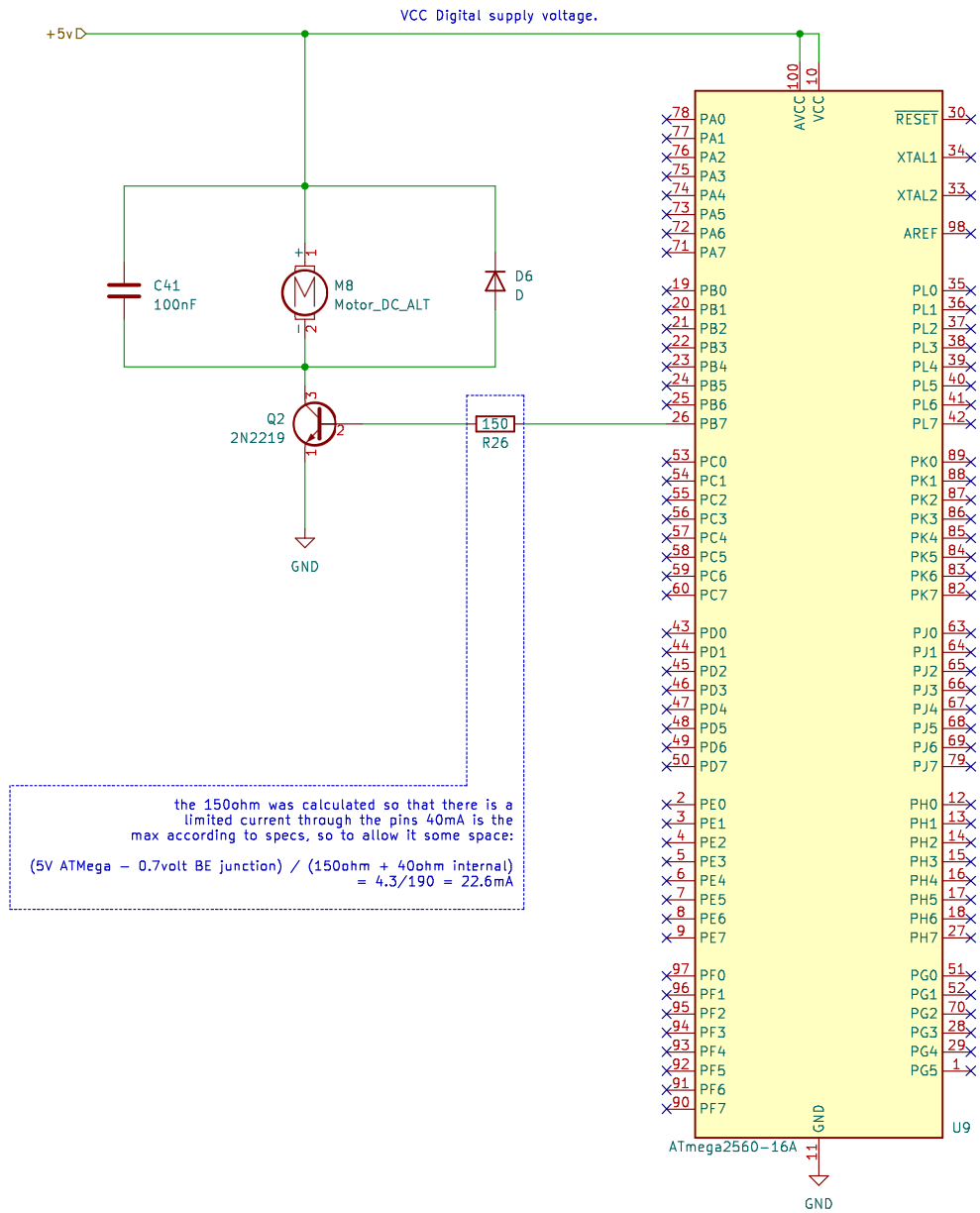

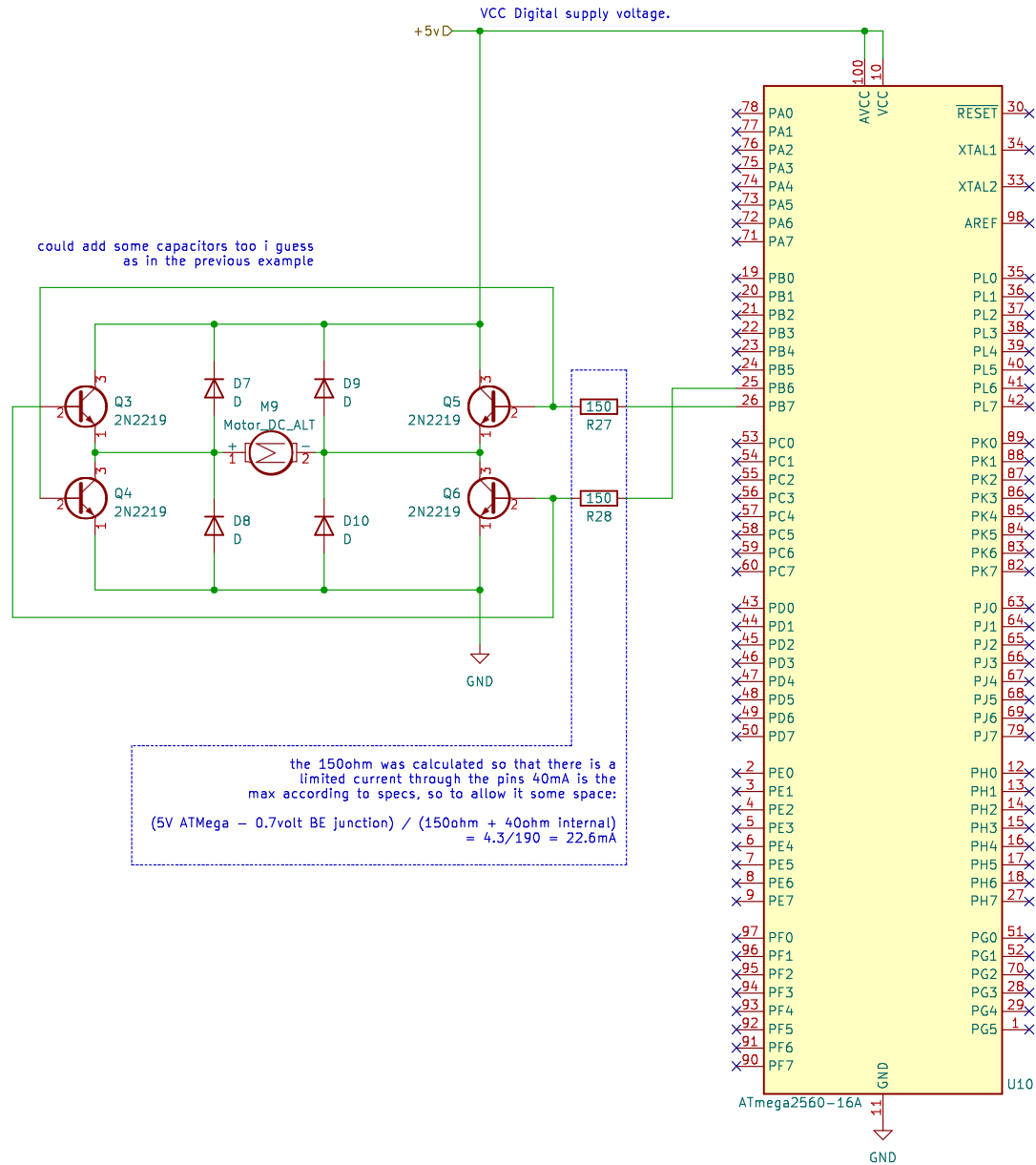the 150ohm was calculated so that there is a limited current through the pins 40mA is the max according to specs, so to allow it some space:
$$(5V \text{ ATmega} - 0.7\text{volt BE junction}) / (150\text{ohm} + 40\text{ohm internal}) = 4.3/190 = 22.6\text{mA}$$



Sheet: /2_3_12/

File: 2_3_12.kicad_sch

Title: High Power Consumption 12


Size: A4


Date:

KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32

Rev:



Id: 14/19

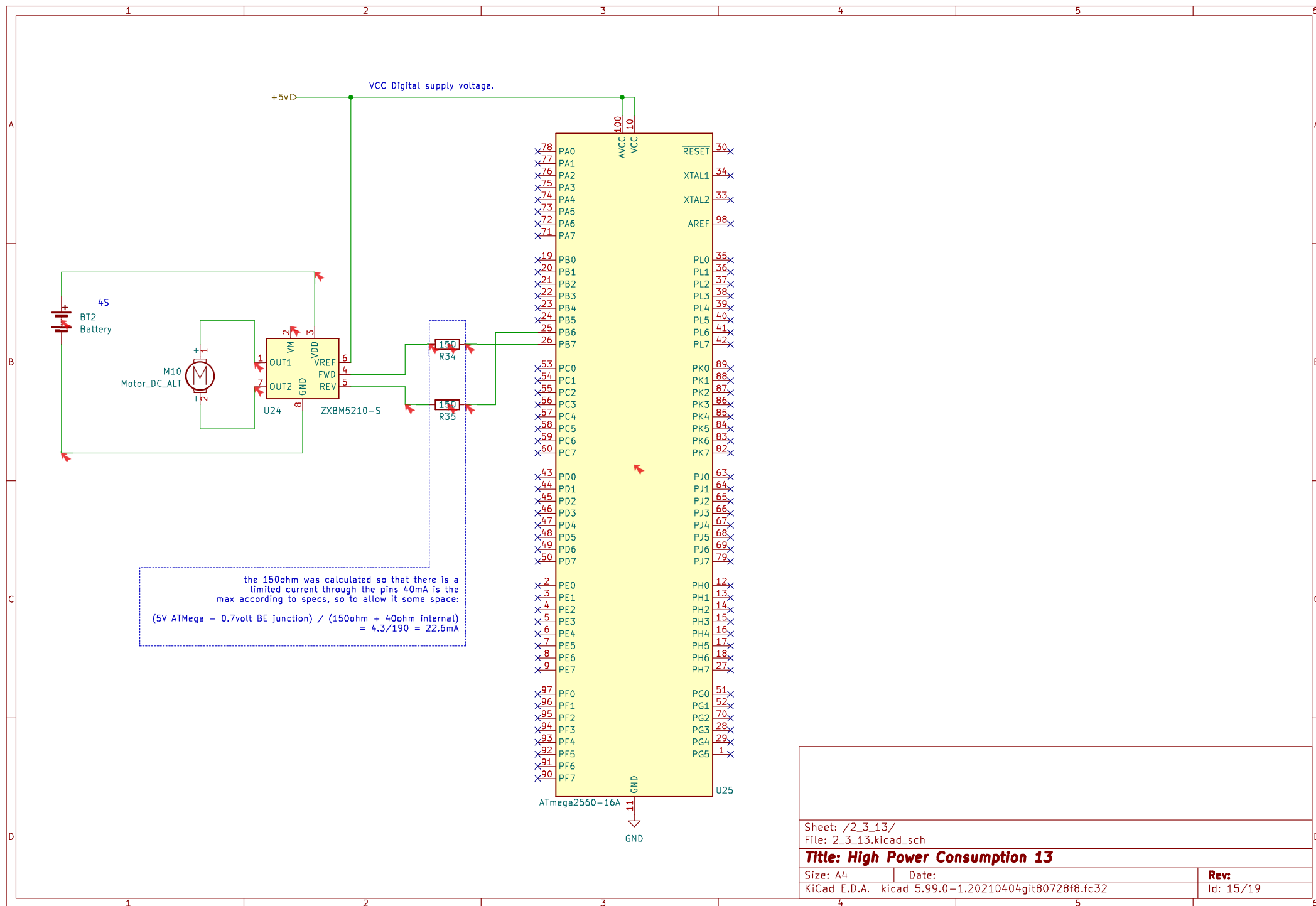


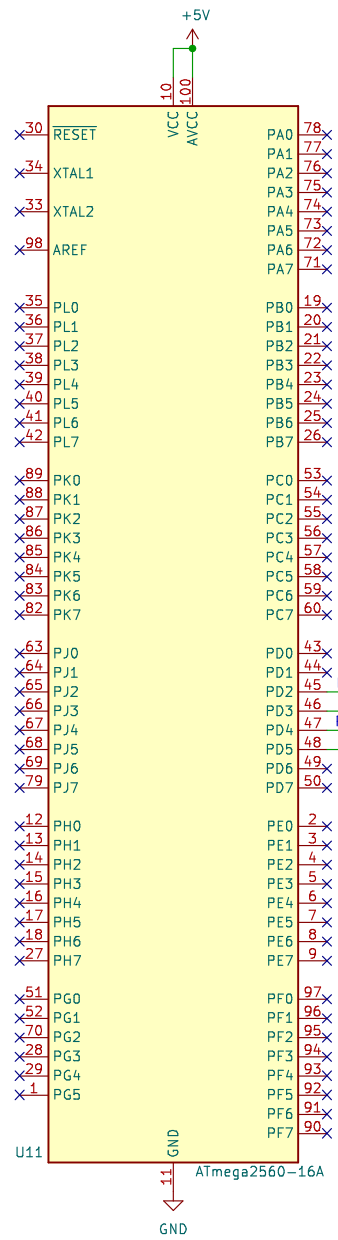


PD5_XCK1 (USART1 External Clock Input/Output)
 PD3_INT3/TXD1 (External Interrupt3 Input or USART1 Transmit Pin)
 PD2_INT2/RXD1 (External Interrupt2 Input or USART1 Receive Pin)

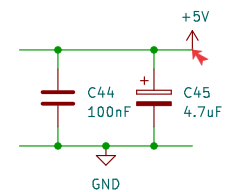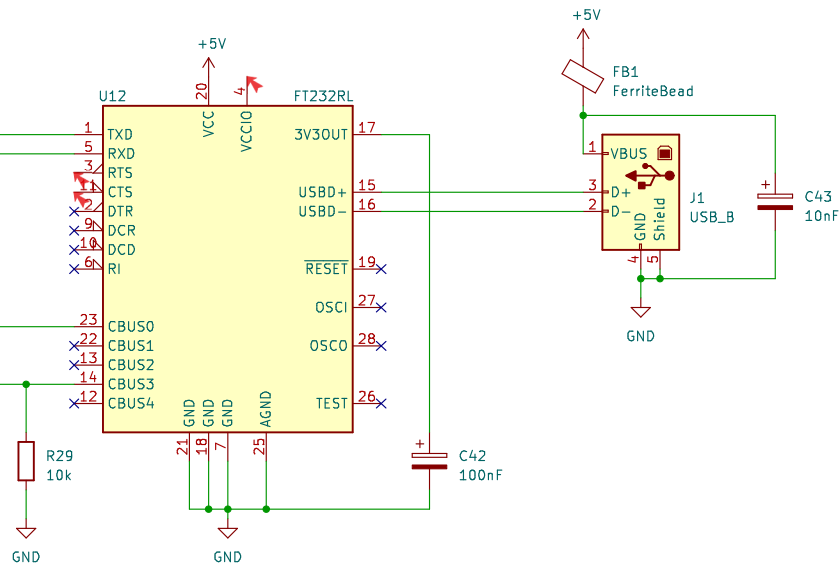http://www.ftdichip.com/Support/Documents/DataSheets/ICs/DS_FT232R.pdf



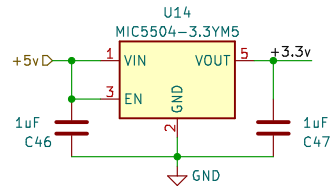


VCC Digital supply voltage.

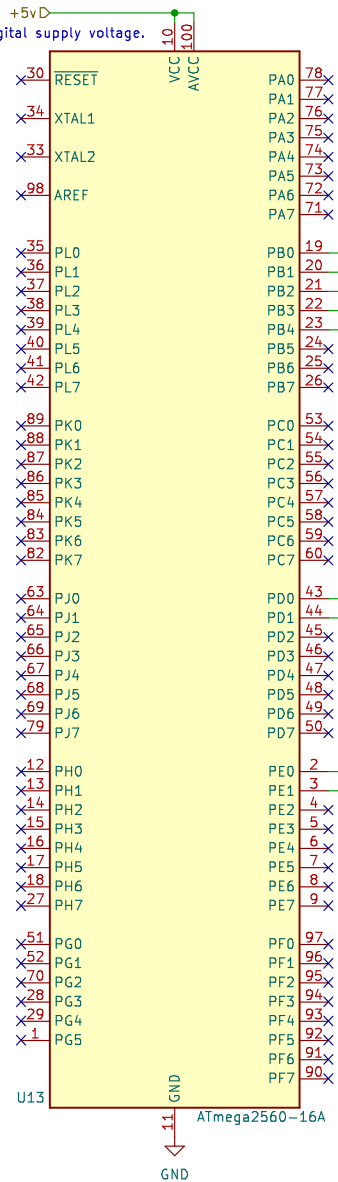

I²C

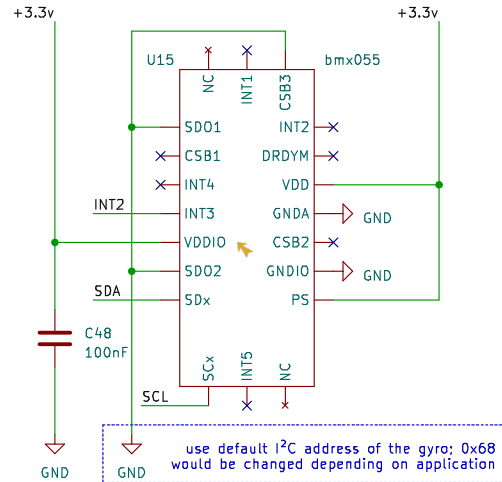PD1 INT1/SDA (External Interrupt1 Input or TWI Serial Data)
PD0 INT0/SCL (External Interrupt0 Input or TWI Serial Clock)



use default I²C address of the gyro; 0x68
would be changed depending on application

VDDIO/VDD supply voltage 1.2...3.6V, input from buck converter

PS Protocol select (GND = SPI, VDDIO=I²C)

INT1 Interrupt pin 1 (accel int #1) -> will be NC
INT2 Interrupt pin 2 (accel int #2) -> will be NC
INT3 Interrupt pin 3 (gyro int #1)
INT4 Interrupt pin 4 (gyro int #2) -> will be NC
INT5 Interrupt pin (magnet) -> will be NC

DRDYM Data ready (magnet) -> will be NC

SD02 SPI serial data out gyro Address selectin I²C mode

SDx I²C: SDA serial data I/O SPI4W: SDI serial data I, SPI 3W: SDA serial data I/O
SCx SPI: serial clock SCK, I²C: serial clock SCL

CSB1 SPI chip select accel

CSB2 SPI chip select gyro

CSB3 SPI chip select magnet. sensor


The communication starts when the CSB (1 or 2) is pulled low by the SPI master and stops when CSB (A.G or M) is pulled high.


SD01 SPI serial data out accel / magnet. sensor I²C-Address[0] of accel / magnet.sensor in I²C mode


ATmega 2560 Digital pins usable for external interrupts:
2, 3, 18, 19, 20, 21 (pins 20 & 21 are not available
to use for interrupts while they are used for I2C communication)

SPI

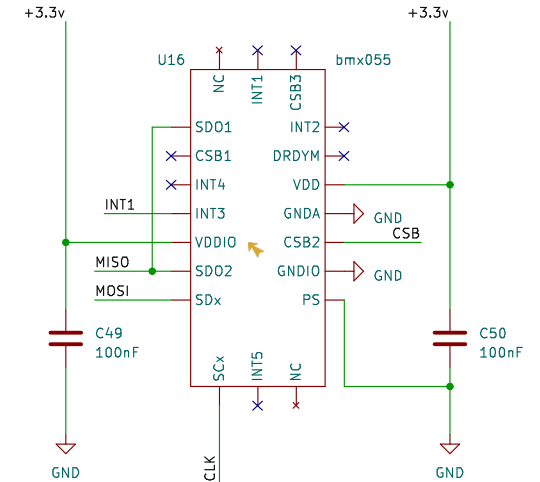
PB3 MISO/PCINT3 (SPI Bus Master Input/Slave Output or Pin Change Interrupt 3)
PB2 MOSI/PCINT2 (SPI Bus Master Output/Slave Input or Pin Change Interrupt 2)
PB1 SCK/PCINT1 (SPI Bus Serial Clock or Pin Change Interrupt 1)
PB0 SS/PCINT0 (SPI Slave Select input or Pin Change Interrupt 0)



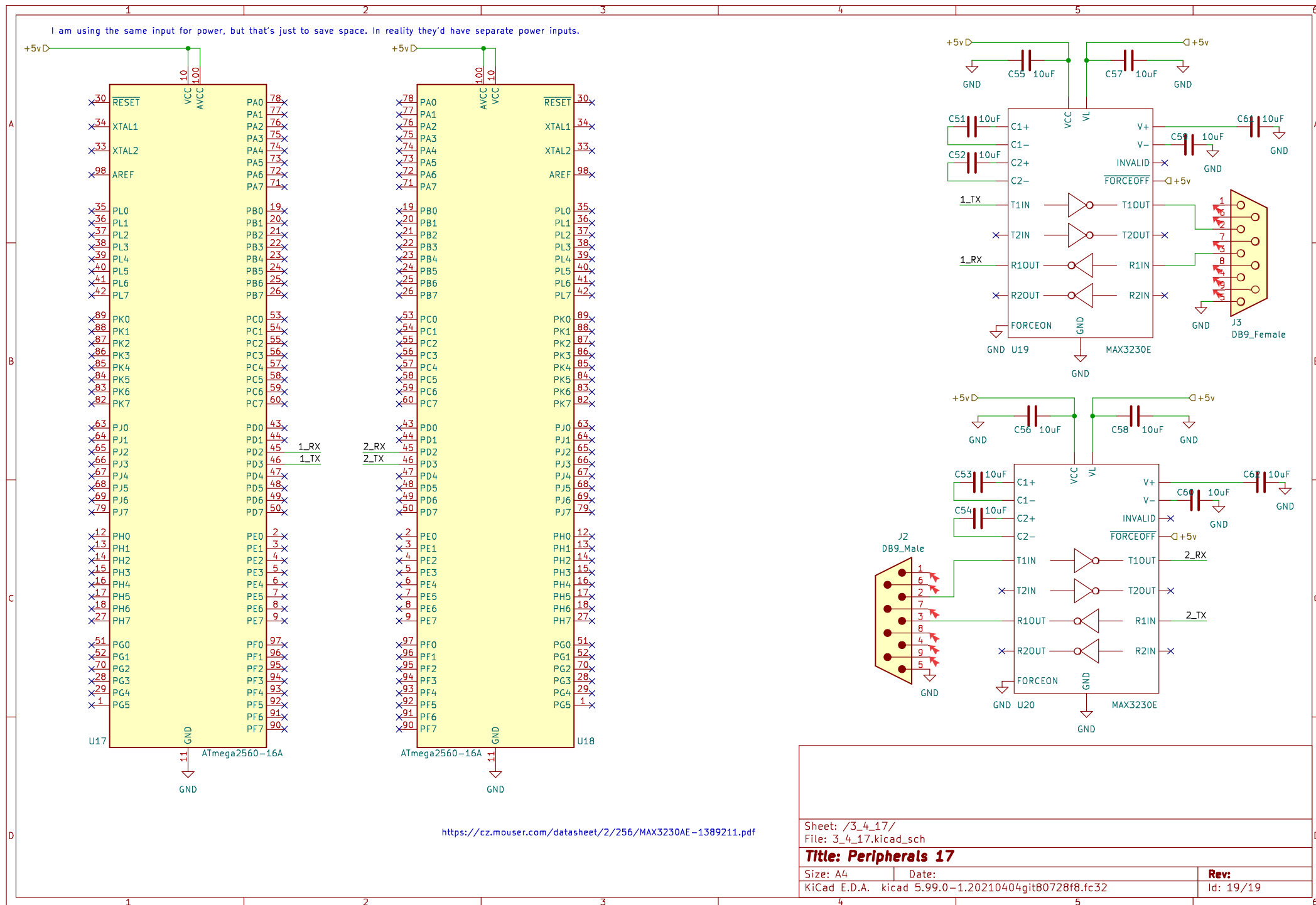

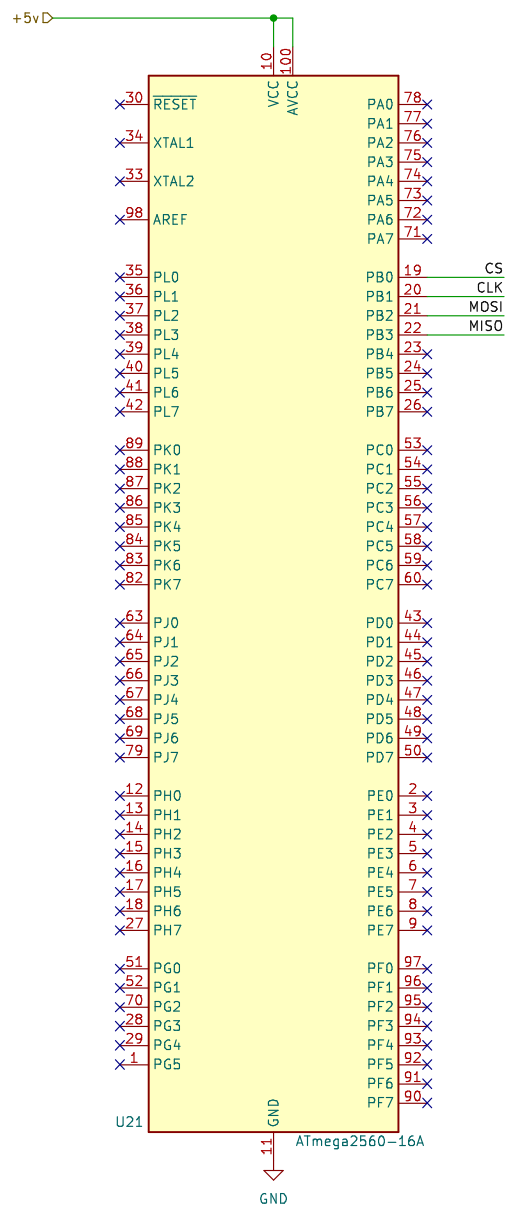
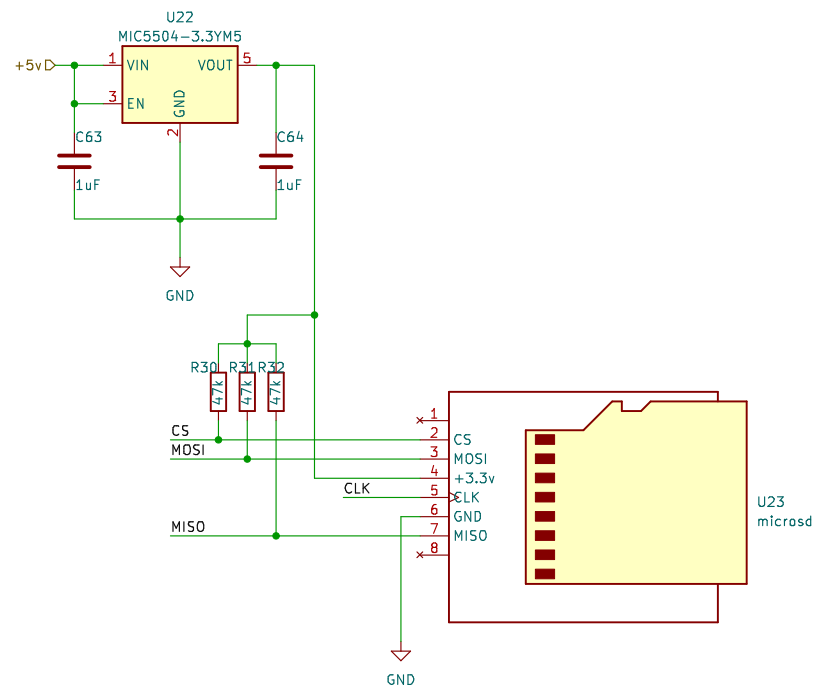
<https://ww1.microchip.com/downloads/en/DeviceDoc/MIC5501-02-03-04-300mA-Single-Output-LDO-in-Small-Packages-DS20006006B.pdf>



Sheet: /3_4_18/		
File: 3_4_18.kicad_sch		
Title: Peripherals 18		
Size: A4	Date:	Rev:
KiCad E.D.A. kicad 5.99.0-1.20210404git80728f8.fc32		Id: 20/19